

Student Name:

Instructor: Mustafa Altun

Student ID:

Date: 24/04/2017

EHB322E Digital Electronic Circuits MIDTERM II

Duration: 120 Minutes

Grading: 1) 30%, 2) 40%, 3) 30%

Exam is in closed-notes and closed-books format; calculators are allowed

For your answers please use the space provided in the exam sheet

GOOD LUCK!


- 1) Consider a Boolean function $f = x_1 x_2 x_3 + \overline{x_1} \overline{x_2} + \overline{x_1} \overline{x_3}$ to be implemented.
Suppose that all NMOS transistors are identical and all PMOS transistors are identical.
Equivalent resistor for an NMOS transistor: $R_N = 12\text{k}\Omega$
Equivalent resistor for a PMOS transistor: $R_P = 24\text{k}\Omega$
Suppose that each circuit node (including outputs) has a capacitance value of **10pF**.

Implement f with “an NMOS and PMOS (CMOS) Pass Transistor Logic” using the ordering of $x_1 - x_2 - x_3$. Find the **minimum number** of transistors needed. Find the **worst case (largest) and best case (smallest) t_{PHL} and t_{PLH}** values (total of 4 values).

- **Hint:** in calculating delay values, use Elmore delay model.

2) Consider a dynamic domino logic circuit shown below.

- Suppose that each transistor has an internal gate capacitor C_G and drain capacitor C_D :
 $C_G = c_{ox} W L$; $C_D = (c_{ox} W L)/2$; $c_{ox} = 0.1 \text{ pF}/\mu\text{m}^2$.
- Equivalent resistor for an NMOS transistor: $R_N = (12\text{k}\Omega) / (W/L)_N$
 Equivalent resistor for a PMOS transistor: $R_P = (24\text{k}\Omega) / (W/L)_P$
- Suppose that all four CMOS inverters are identical with same W_{N-In} and W_{P-In} values.
- $W_{N1} = W_{N2} = W_{N3} = 1\mu$, $W_{P1} = 2\mu$, $W_{P-In} = 2\mu$, $W_{N-In} = 1\mu$, $L = 1\mu$ for all transistors,
 $V_{TN} = |V_{TP}| = 1\text{V}$, $V_{DD} = 5\text{V}$.

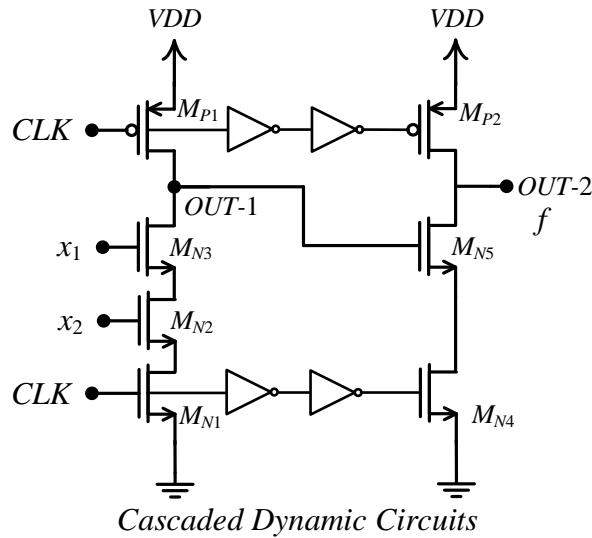

- Derive a Boolean expression of f in terms of x_1 and x_2 in evaluation phase.
- Find the value of W_{N5} if $V_{OUT-1} = 4.5\text{V}$ as a result of charge sharing (problem).
- Find the **worst case** t_{PHL} for OUT-1. Suppose that all input transitions happen in pre-charge phase and each circuit node has an initial voltage value of either 0V or 5V.
- Find the values of W_{P2} and W_{N4} if the worst case t_{PHL} for OUT-1, calculated in c), is same as the clock delay (total delay of two cascaded inverters).

3) Consider the circuit.

- Suppose that all NMOS transistors are identical and all PMOS transistors are identical.
Equivalent resistor for an NMOS transistor: $R_N = 8\text{k}\Omega$
Equivalent resistor for a PMOS transistor: $R_P = 24\text{k}\Omega$
 - Suppose that each circuit node (including outputs) has a capacitance value of **10pF**.
- a) Derive a Boolean expression for the output ***F*** in terms of inputs **A** and **B**.
- b) Calculate the worst case and the best case propagation delays, **t_{PLH}** and **t_{PHL}** values (total of 4 values).

