

October 3, 2016
Due to: October 17, 2016

Basic of Electrical Circuits Homework#1

- 1- a) Find all the possible trees of the graph in Fig. 1.
b) One of the possible trees is given by: {1, 2, 3, 4}. Find the fundamental loop and cut-set equations related with this tree. c) Show the validity of the following equation: $B_1 = -Q_1^T$.

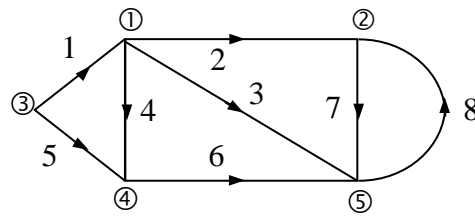


Fig. 1

2. Sketch the circuit graph of the circuit below.

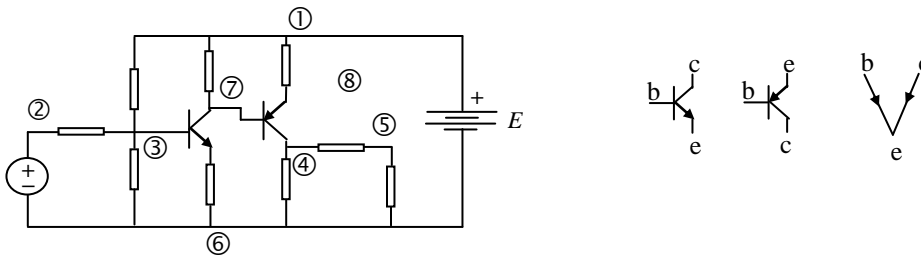


Fig. 2