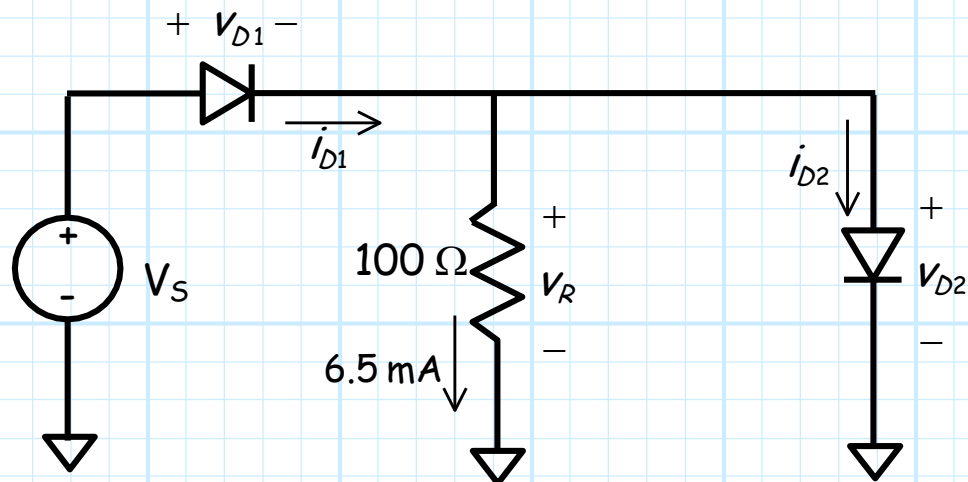



# Example: A Junction Diode Circuit

Consider the following circuit with two junction diodes:



The diodes are identical, with  $n = 1$  and  $I_S = 10^{-14}\ \text{A}$ .

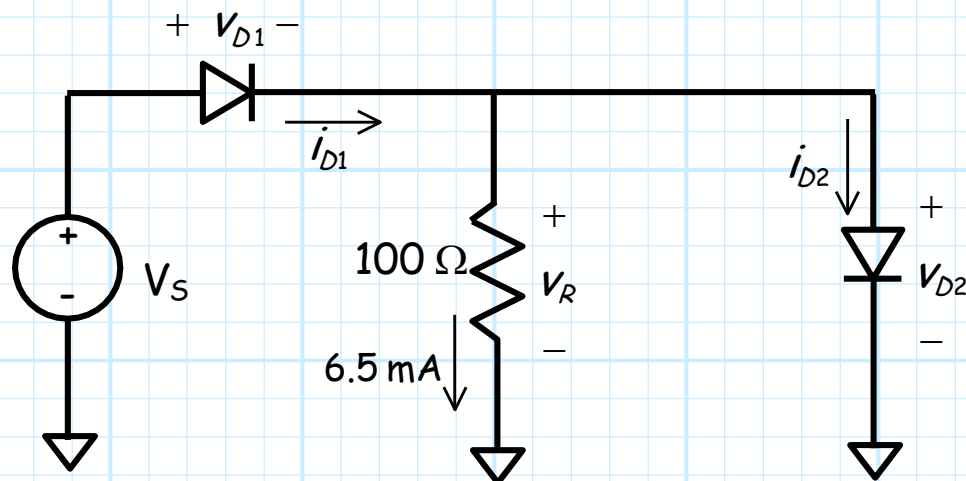**Q:** *If the current through the resistor is  $6.5\ \text{mA}$ , what is the voltage of source  $V_S$ ??*



1) If 6.5 mA flows through a 0.1 K resistor, the voltage across that resistor is:

$$V_R = 0.1 (6.5) = 0.65 V$$

2) If the voltage across the resistor is 0.65 V, then the voltage across the diode  $D_2$ , which is **parallel** to the resistor, is the **same** value:


$$V_{D2} = V_R = 0.65 V$$

3) If we know the **voltage** across a p-n junction diode, then we also know its **current** !

$$i_{D2} = I_S \exp \frac{V_{D2}}{nV_T} = 10^{-14} \exp \frac{0.650}{0.025} = 1.96 \text{ mA}$$

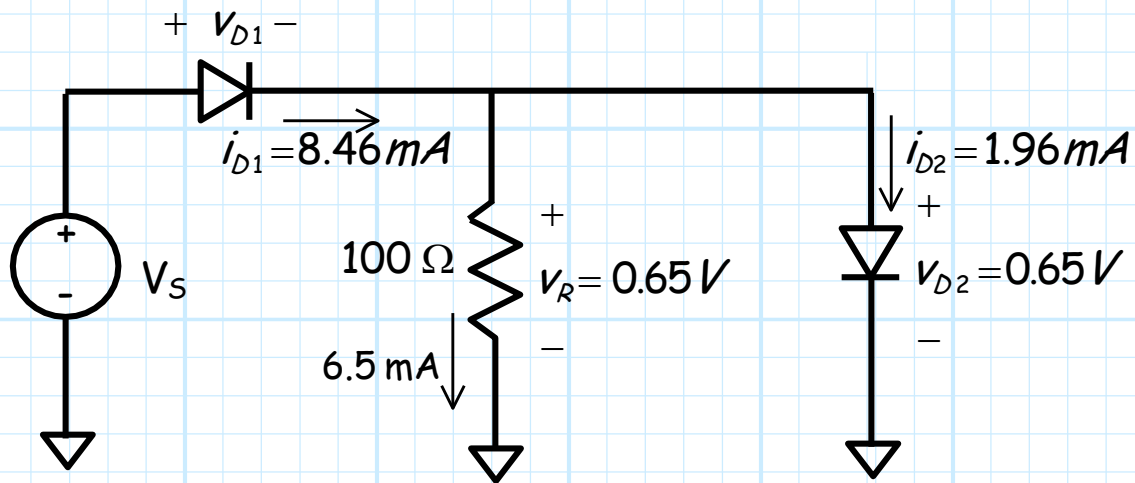4) If we know  $i_{D2}$  and the current through the resistor, we know (using KCL) the current through  $D_1$ :

$$\begin{aligned} i_{D1} &= 6.5 + i_{D2} \\ &= 6.5 + 1.96 \\ &= 8.46 \text{ mA} \end{aligned}$$




5) If we know the **current** through a junction diode, then we can find the **voltage** across it:

$$v_{D1} = nV_T \ln \frac{i_{D1}}{I_S} = 0.025 \ln \frac{0.00846}{10^{-14}} = 0.69 \text{ V}$$

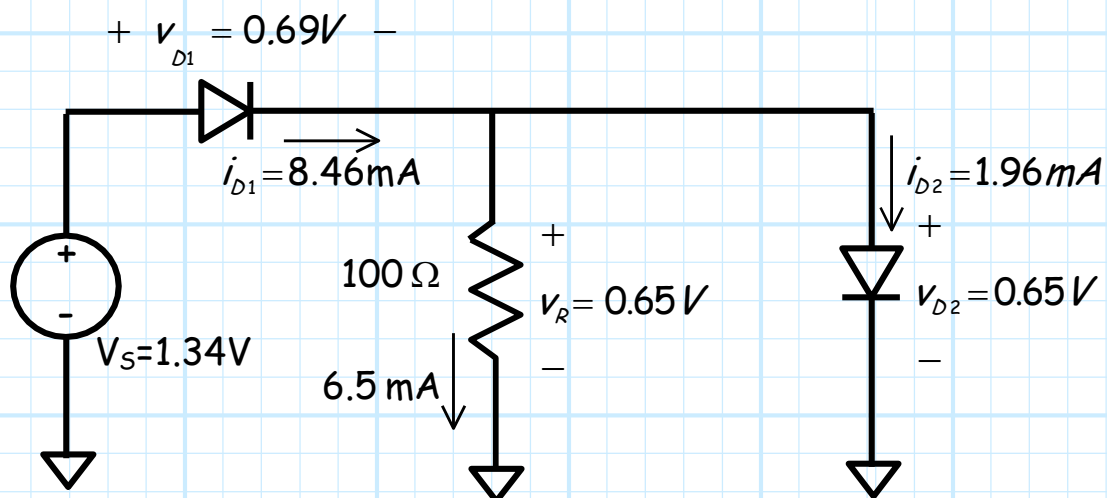
6) Finally, if we know  $v_{D1}$  and  $v_{D2}$ , we can find  $V_S$  using KVL:

$$V_S = v_{D1} + v_{D2} = 0.69 + 0.65 = 1.34 \text{ V}$$


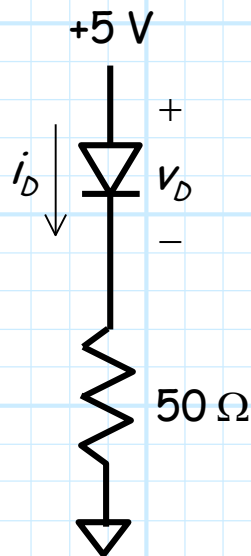
# Example: Junction Diode Models

Consider the **junction** diode circuit, where the junction diode has device parameters  $I_S = 10^{-12} \text{ A}$ , and  $n=1$ :






I **numerically** solved the resulting transcendental equation, and determined the **exact** solution:


$$i_D = 87.40 \text{ mA}$$

$$v_D = 0.630 \text{ V}$$

Now, let's determine **approximate** values using diode **models**!

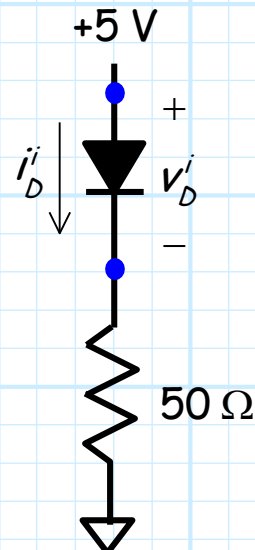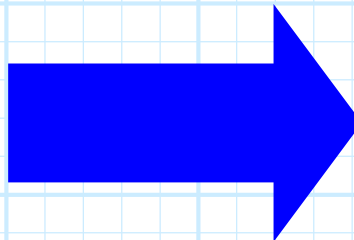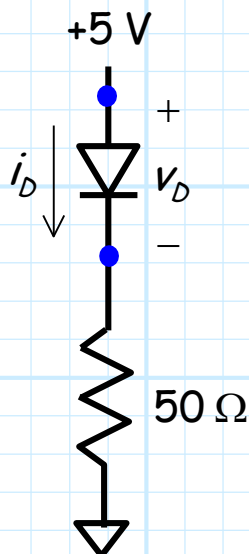First, let's try the **ideal diode model**.



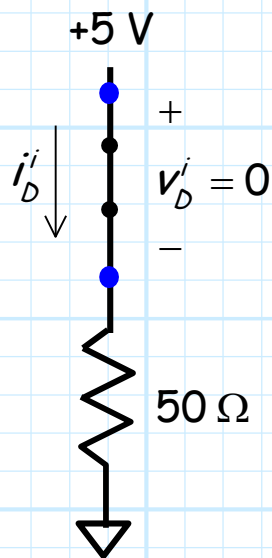

Assume **IDEAL** diode is "on".

Enforce  $v_D^i = 0$ .

Analyze the **IDEAL** diode circuit.  
From KVL:

We therefore can **approximate** the **junction diode** current as the current through the ideal diode **model**:

$$i_D \approx i_D^i = 100 \text{ mA}$$





And **approximate** the **junction** diode voltage as the voltage across the ideal diode **model**:

$$v_D \approx v_D^i = 0$$

**Compare** these approximations to the **exact** solutions:

$$i_D = 87.4 \text{ mA} \quad \text{and} \quad v_D = 0.630 \text{ V} \quad \text{Close, but we can}$$

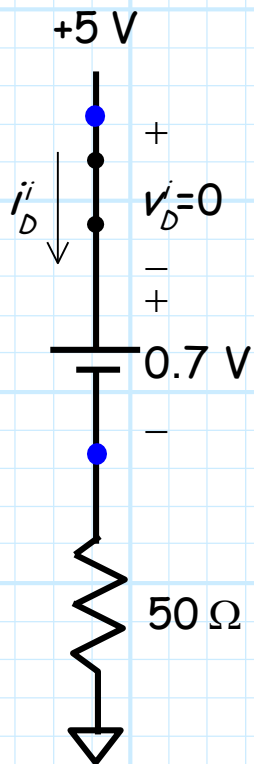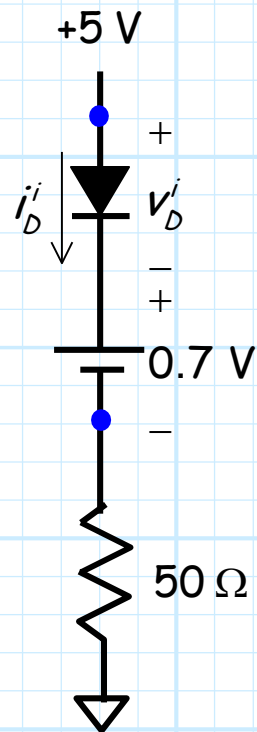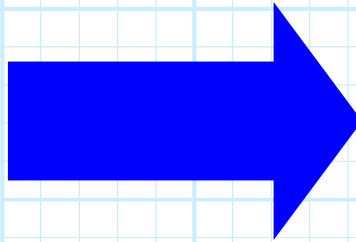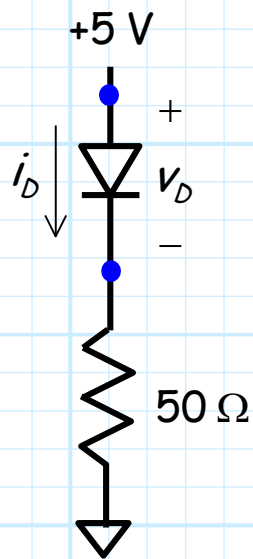do better! Let's use the 'Modified diode model'.



Assume **IDEAL** diode is "on".

Enforce  $v_D^i = 0$ .

Analyze the **IDEAL** diode circuit.  
From KVL:

We therefore can **approximate** the **junction** diode current as the current through the 'Modified diode model **model**:

$$i_D \approx i_D' = 86.0 \text{ mA}$$

And **approximate** the **junction** diode voltage as the voltage across the 'Modified diode model **model**:


$$\begin{aligned} v_D &\approx v_D' + 0.7 \\ &= 0.0 + 0.7 \\ &= 0.7 \text{ V} \end{aligned}$$

Compare these approximations to the **exact** solutions:

$$i_D = 87.4 \text{ mA} \quad \text{and} \quad v_D = 0.630 \text{ V}$$

# Example: Diode Small-Signal Analysis

Consider the circuit:

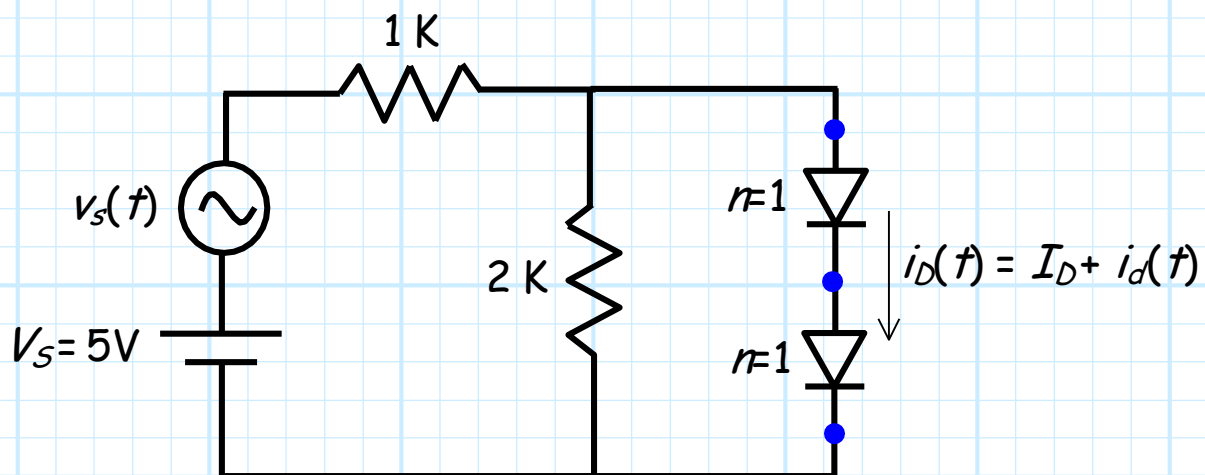


**Q:** If  $v_s(t) = 0.01 \sin \omega t$ , what is  $i_d(t)$ ?

**A:** Follow the small-signal analysis steps!


**Step 1:** Complete a D.C. Analysis

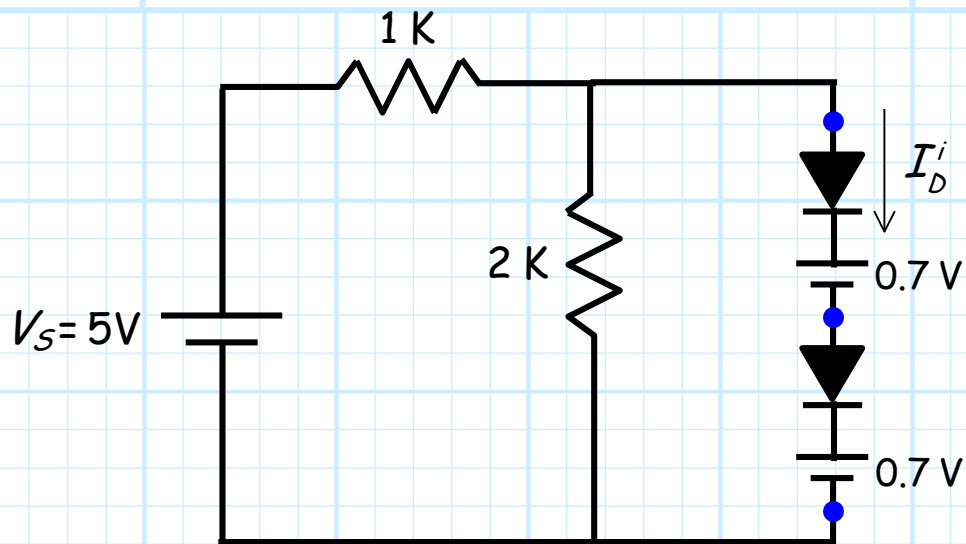Turn **off** the small-signal source and replace the junction diodes with the 'modified diode model' model.





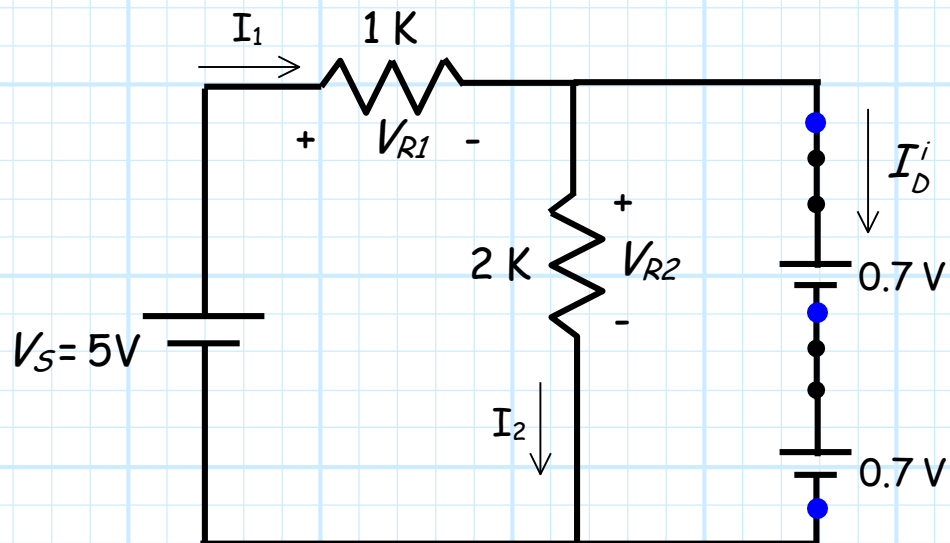**Assume** the ideal diodes are "on", **enforce** with short circuits.



Now analyze the D.C. circuit:

From KVL  $V_{R2} = 0.7 + 0.7 = 1.4\text{ V}$

$$\therefore I_2 = \frac{V_{R2}}{2} = 0.7\text{ mA}$$

From KVL:  $V_{R1} = 5.0 - V_{R2} = 5.0 - 1.4 = 3.6\text{ V}$

Thus from Ohm's Law:  $I_1 = \frac{V_{R1}}{1} = 3.6 \text{ mA}$

And finally from KCL: 
$$\begin{aligned} I_D^i &= I_1 - I_2 \\ &= 3.6 - 0.7 \\ &= 2.9 \text{ mA} \end{aligned}$$

Now **checking** our result:

$$I_D^i = 2.9 \text{ mA} > 0 \quad \checkmark$$

Therefore our estimate of the D.C. diode current is:


$$I_D = I_D^i = 2.9 \text{ mA}$$

**Step 2:** Calculate the diode small-signal resistance  $r_d$ :

$$r_d = \frac{nV_T}{I_D} = \frac{0.025}{0.0029} = 8.6 \Omega$$

Note since the junction diodes are **identical**, and since each has the **same** current  $I_D = 2.9 \text{ mA}$  flowing through it, the small-signal resistance of each junction diode is the **same** ( $r_d = 8.6 \Omega$ ).

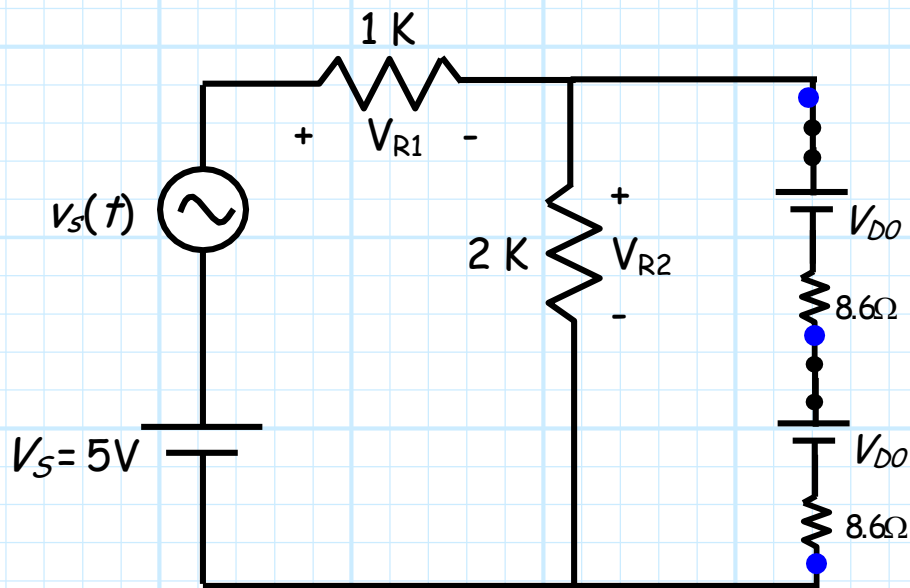
**Step 3:** Replace junction diodes with **small-signal model**



**Step 4:** Determine the **small-signal circuit**.


This means turn off the 5V source **and** the  $V_{D0}$  sources in the 'modified diode **model**' !

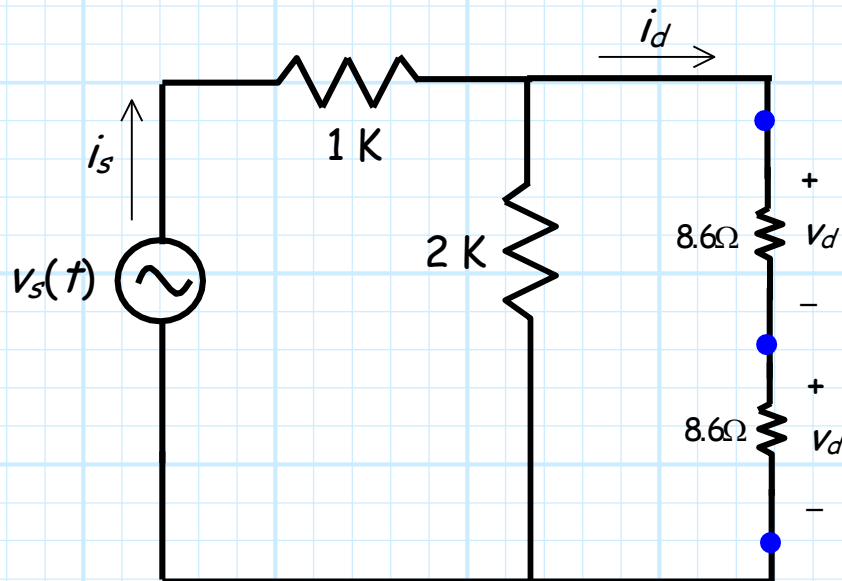After turning off all DC sources, we are left with our **small-signal circuit**:



**Step 5:** Analyze the small-signal circuit.

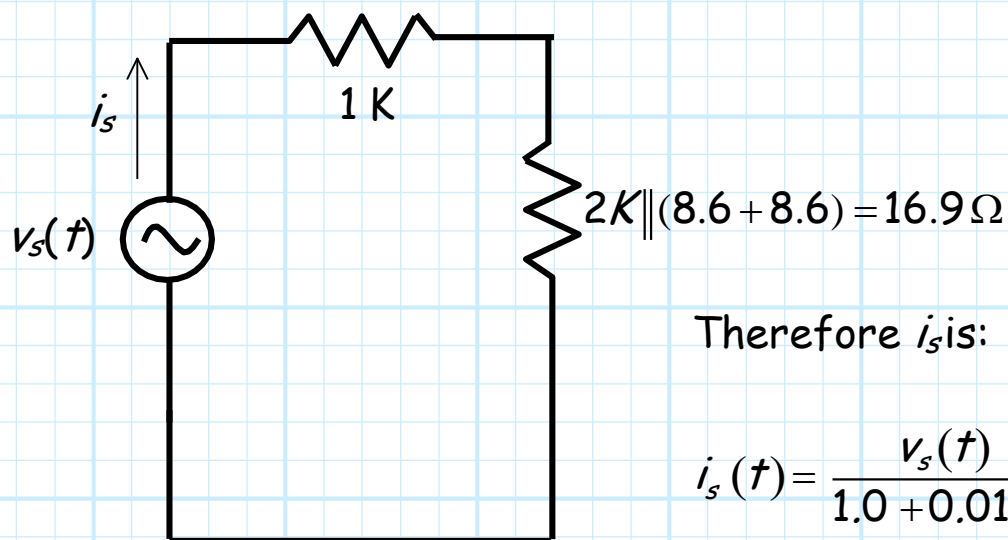Combining the parallel resistors, we get:



Therefore  $i_s$  is:

$$i_s(t) = \frac{v_s(t)}{1.0 + 0.0169}$$

= ...

We can now find  $i_d$  using **current division**:

