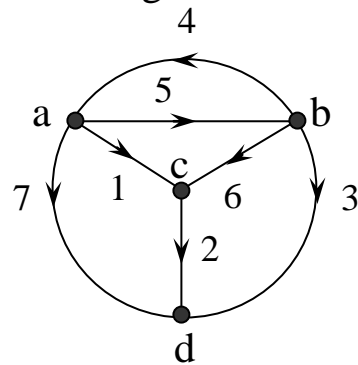




# Graph Theory

A structure consisting of vertices and edges






number of vertices=4  
number of edges=7


Element graph

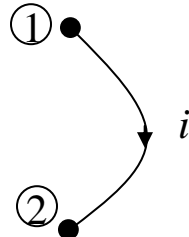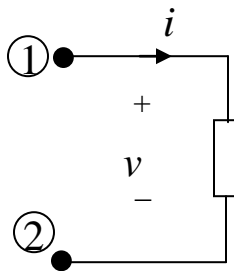



Passive sign convention  
should be met

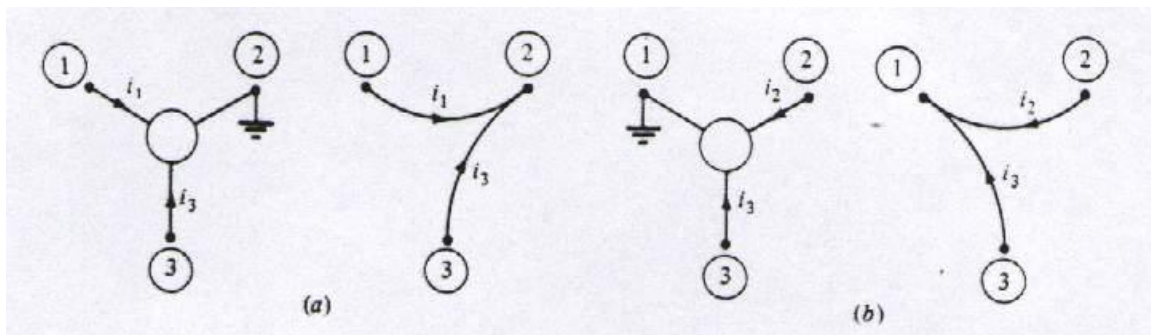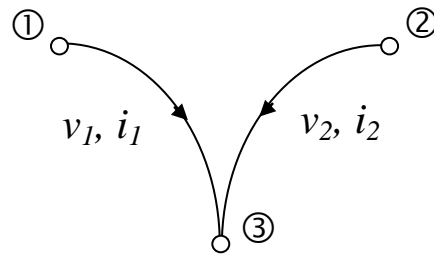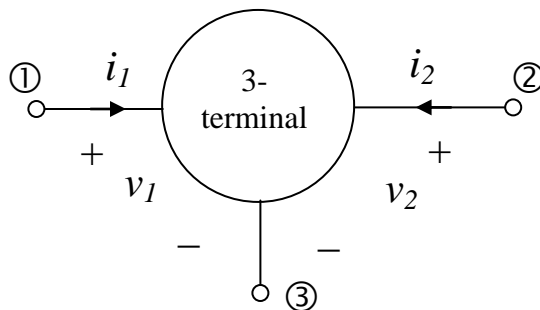


## Element graph of an n-terminal

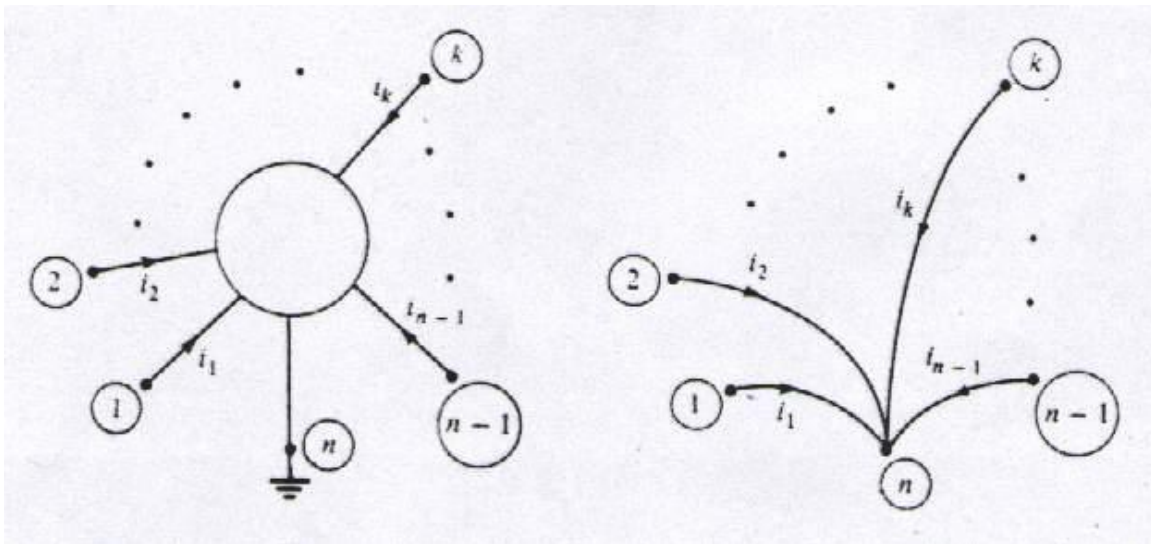


## Two-port and multi-port elements

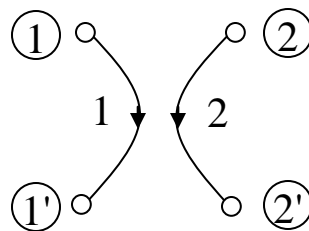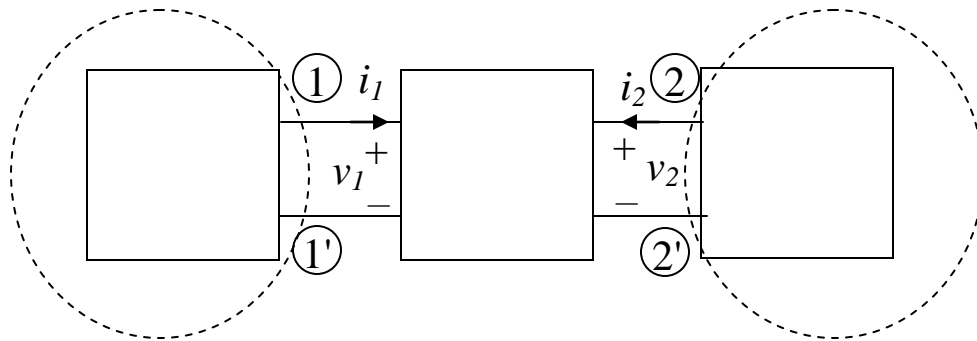


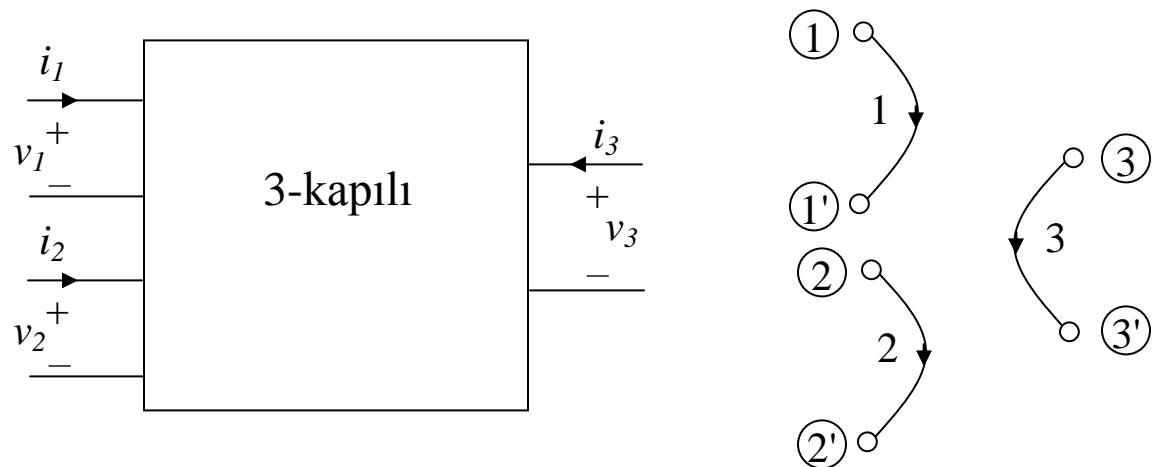

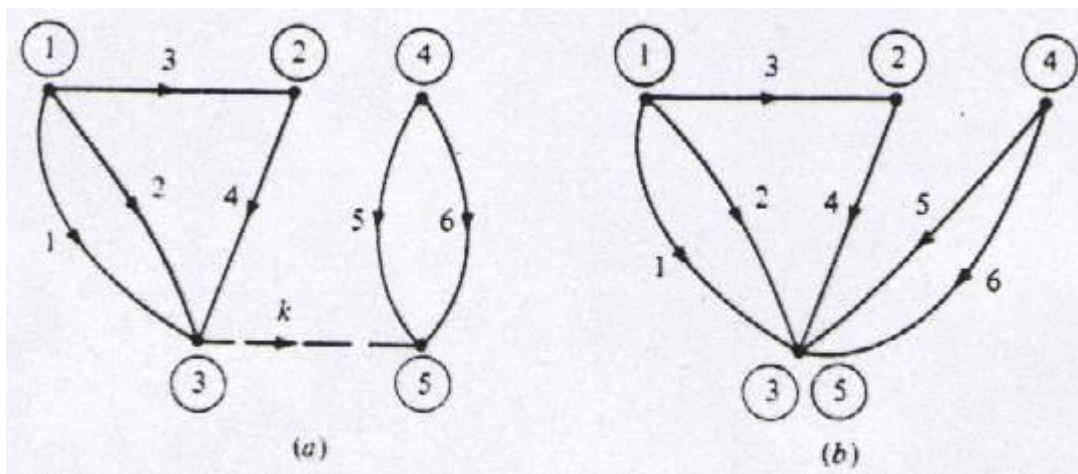The graph of a 2-port element is disjoint. However any disjoint graph can be converted into a connected graph as shown below.



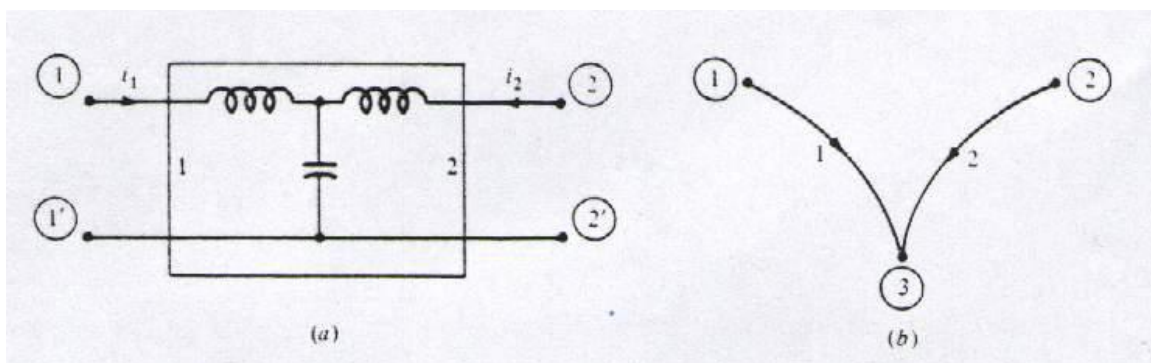The subcircuit below can be considered either a 2port or 3-terminal.




**Circuit graph:** A graph is a pictorial structure which represents the interconnections of the elements in an electric circuit.

**Edge:** A directed line which represents a connection between vertices

**Vertex (node, point):** The edges of an edge

**degree (of a vertex):** the number of edges connected to a vertex

$\delta(d_i)=4$

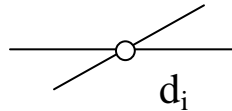

**An isolated vertex is** a vertex with  $\delta=0$

In a graph with  $n_e$  elements and  $n$  vertices, the sum of degrees of all vertices equals to  $2 n_e$ .

**Subgraph** is graph formed from a subset of the vertices and edges of a given graph.

**Path** is a sequence of vertices and edges, with both endpoints of an edge appearing adjacent to it in the sequence

**A connected graph** is one in which each pair of vertices forms the endpoints of a path. Otherwise, it is disjoint graph.

**Loop** is a path whose endpoints are the same vertex. Degrees of all vertices in a loop is 2.


**Tree:** A tree is a connected and acyclic subgraph which contains all the vertices of the given graph.

Provided that the graph has  $n_e$  edges and  $n_d$  vertices, in a tree,

1. the number of edges is  $n_e - 1$ .
2. There is one only one path interconnecting each pair of vertices.
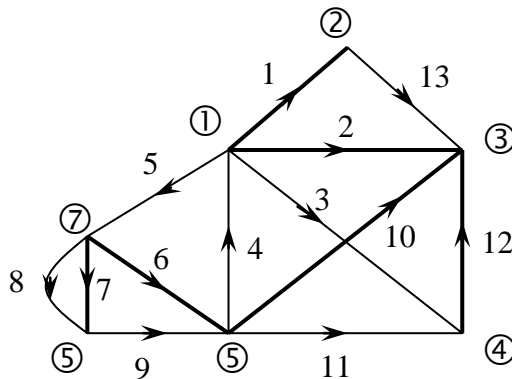
### Fundamental Loop set:

Each co-tree of a tree and some branched define a loop. For a given tree, there is  $n_e - n_d + 1$  such loops. These loop constitute fundamental loop set.



Fundamental loop sets:

$\{8, 7\}$

$\{9, 7, 6\}$

$\{3, 12, 2\}$

$\{13, 1, 2\}$

$\{11, 10, 12\}$


toplam  $n_e - n_d + 1 = 13 - 7 + 1 = 7$

**Cut-set:** Some elements in graph  $G$  satisfying the followings constitute a cut-set.

- a) After removal of these elements, graph is split into two parts.
- b) Any subset of these elements satisfy a).
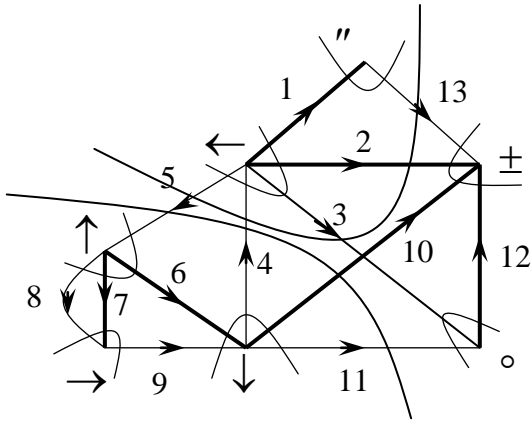
### Fundamental cut-set:

For a given tree, each of the branches constitutes a cut-set with only some branches of the tree. This cut-set is called fundamental cut-set.




Connected graph

$$n_e = 13 \Rightarrow \text{dal } n_d - 1 = 7 - 1 = 6$$

$$n_d = 7 \Rightarrow \text{kiriş } n_e - n_d + 1 = 7$$

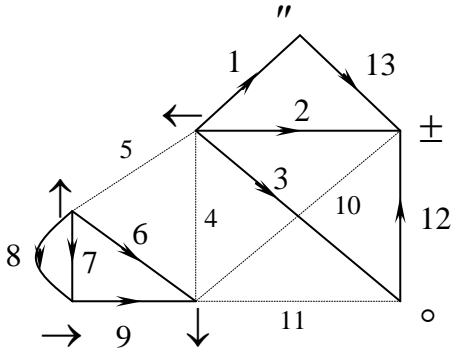- Co-tree elements  $G_K = \{3, 4, 5, 8, 9, 11, 13\}$
- Tree  $G_T = \{1, 2, 6, 7, 10, 12\}$



$\{5, 4, 10, 11\}$  is a cut-set

- Cut-set  $G_{DK} = \{1, 2, 3, 4, 5\}$

# Graph Matrices

## 1. Fundamental Loop Matrix

Fill in the entries of the matrix  $\mathbf{B}_t=[b_{ij}]$  as follows:


$$b_{ij}=0; \quad \text{jth element is not included in the ith fundamental loop,}$$

$b_{ij}=1$ ;  $j$ th element is included in the  $i$ th fundamental loop, and the element is in the same orientation as the loop,

$b_{ij}=-1$ ;  $j$ th element is included in the  $i$ th fundamental loop, and the element is in the opposite orientation as the loop.

(the orientation of a loop is the same as that of the co-tree)

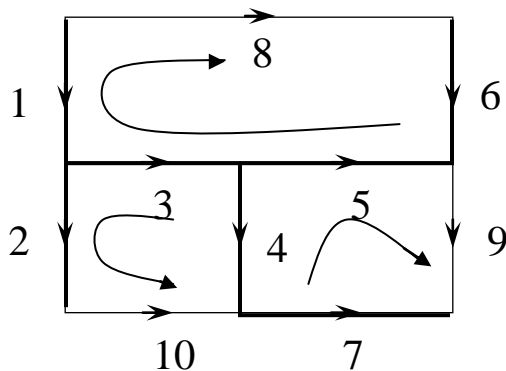
The matrix  $\mathbf{B}_t$ , thus obtained is called fundamental loop matrix.



Dimensions of matrix  $B_t$  is  $(n_e - n_d + 1) \times (n_e)$

$$\mathbf{B}_t = \begin{array}{c} (8) \\ (9) \\ (10) \end{array} \left[ \begin{array}{cccccccc|ccc} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 \\ -1 & 0 & -1 & 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & -1 & 0 & 1 & 0 \\ 0 & 1 & -1 & -1 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right]$$
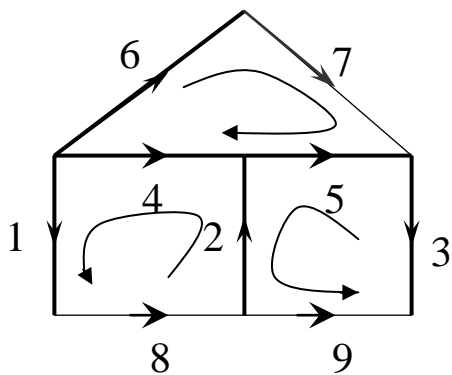
$$\mathbf{B}_t = [ \underbrace{\mathbf{B}_1}_{n_d-1} \quad \vdots \quad \underbrace{\mathbf{U}}_{n_e-n_d+1} ] \quad n_e-n_d+1$$



$$\mathbf{B}_t = \begin{array}{c} (7) \\ (8) \\ (9) \end{array} \begin{array}{c} \left| \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \\ 0 & 0 & 0 & -1 & -1 & 1 \\ 1 & 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & -1 & 0 & -1 & 0 \end{array} \right| \end{array} \begin{array}{c} \underbrace{\hspace{10em}}_{\text{branches}} \quad \underbrace{\hspace{10em}}_{\text{co-tree edges}} \end{array}$$

$$\mathbf{B}_t = [ \quad \mathbf{B}_1 \quad \vdots \quad \mathbf{U} \quad ]$$

Rank  $\{ \mathbf{B}_t \} = n_e - n_d + 1 = \text{number of co-trees} = \text{number of fundamental loops}$



## 2. Fundamental Cut-Set Matrix

For each fundamental cut-set in graph  $G$ , construct the fundamental cut-set matrix  $\mathbf{Q}_f = [q_{ij}]$  according to the following steps:


$q_{ij} = 0$ ;  $j$ th element is not included in the set of  $i$ th fundamental cut,  
cut,

$q_{ij} = 1$ ;  $j$ th element is included in the set of  $i$ th fundamental cut and it is in the same orientation as the cut-set.

$q_{ij} = -1$ ;  $j$ th element is included in the set of  $i$ th fundamental cut and it is in the opposite orientation as the cut-set.

(the direction of the cut set is chosen as the direction of the branch)

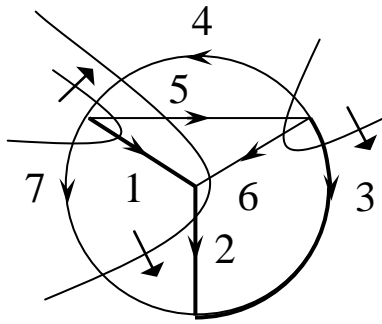**The orientation of cut-set is the same as that of co-tree element and is taken positive.**



$$\mathbf{Q}_t = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} (1) \\ (2) \\ (3) \end{matrix} & \left| \begin{array}{cccccc} 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 1 & 0 & -1 & 1 & -1 & 1 \\ 0 & 0 & 1 & 1 & -1 & 1 & 0 \end{array} \right| \end{matrix}$$

$\underbrace{\hspace{10em}}_{\text{branches}} \quad \underbrace{\hspace{10em}}_{\text{co-tree edges}}$

$$\mathbf{Q}_t = \left[ \underbrace{\mathbf{U}}_{n_d-1} \quad \vdots \quad \underbrace{\mathbf{Q}_1}_{n_e-n_d+1} \right] \quad n_d-1$$

$$\mathbf{B}_t = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} (4) \\ (5) \\ (6) \\ (7) \end{matrix} & \left| \begin{array}{cccccc} 1 & 1 & -1 & 1 & 0 & 0 & 0 \\ -1 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 & 0 \\ -1 & -1 & 0 & 0 & 0 & 0 & 1 \end{array} \right| \end{matrix}$$

$\underbrace{\hspace{10em}}_{\mathbf{B}_1} \quad \underbrace{\hspace{10em}}_{\mathbf{U}}$

$$\mathbf{Q}_1 = -\mathbf{B}_1^T$$

$$\mathbf{B}_1 = -\mathbf{Q}_1^T$$


Property:  $\mathbf{Q}_t \mathbf{B}_t^T = \mathbf{0} \Leftrightarrow \mathbf{B}_t \mathbf{Q}_t^T = \mathbf{0}$

$$\begin{aligned} \mathbf{Q}_t \mathbf{B}_t^T &= [\mathbf{U} \quad \mathbf{Q}_1] [\mathbf{B}_1 \quad \mathbf{U}]^T = [\mathbf{U} \quad \mathbf{Q}_1] \begin{bmatrix} \mathbf{B}_1^T \\ \mathbf{U} \end{bmatrix} \\ &= \mathbf{B}_1^T + \mathbf{Q}_1 = \mathbf{B}_1^T + (-\mathbf{B}_1^T) = \mathbf{0} \end{aligned}$$
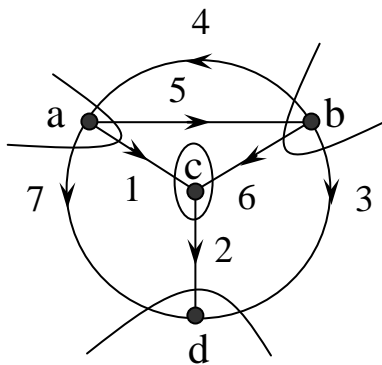
## Incidence Matrix

Choose all the cut-sets in such a way that one of the parts related to the cut-set consists of a single vertex. The fundamental loop matrix of this specific cut-set is the node incidence matrix,  $A$ .

✓ Dimensions of  $A$  is  $(n_d) \times (n_e)$



$$\bar{A} = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} (a) \\ (b) \\ (c) \\ (d) \end{matrix} & \left| \begin{array}{ccccccc} 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 & -1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 0 & -1 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & -1 \end{array} \right| \end{matrix}$$

#### 4. Reduced incidence matrix, $\mathbf{A}$

The matrix obtained by removing one of the rows of  $\bar{\mathbf{A}}$  is called reduced incidence matrix

$$\mathbf{A} = \begin{array}{c|cccccc} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ \hline \text{(a)} & 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ \text{(b)} & 0 & 0 & 1 & 1 & -1 & 1 & 0 \\ \text{(c)} & -1 & 1 & 0 & 0 & 0 & -1 & 0 \\ \hline \text{(d)} & 0 & -1 & -1 & 0 & 0 & 0 & -1 \end{array} \quad \text{rank } \mathbf{A} = n_d - 1$$


Reduced incidence matrix is a full rank matrix.

**Property:**

$$\checkmark \quad \mathbf{A} = \left[ \underbrace{\mathbf{A}_1}_{\text{branches}} \quad \vdots \quad \underbrace{\mathbf{A}_2}_{\text{co-trees}} \right] \quad n_d - 1 \Rightarrow \quad \mathbf{A}_1^{-1} \mathbf{A} = \mathbf{Q}_T$$

$$\mathbf{A}_1^{-1} \mathbf{A} = [\mathbf{U} : \mathbf{A}_1^{-1} \mathbf{A}_2] = \mathbf{Q}_T = [\mathbf{U} : \mathbf{Q}_1]$$
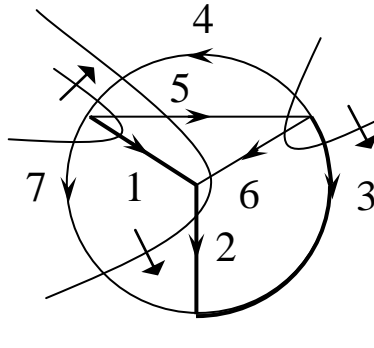
$$\Rightarrow \quad \mathbf{Q}_1 = \mathbf{A}_1^{-1} \mathbf{A}_2$$



$$\mathbf{A} = \begin{array}{c} \text{(a)} \\ \text{(b)} \\ \text{(c)} \end{array} \begin{array}{c} 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \\ \left| \begin{array}{ccc|ccc} 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 & -1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 0 & -1 & 0 \end{array} \right| \end{array}$$

dallar ( $\mathbf{A}_1$ )      kırışlar ( $\mathbf{A}_2$ )

$$\mathbf{A} = [\mathbf{A}_1 \quad \vdots \quad \mathbf{A}_2]$$

$$\mathbf{A}_1 = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 0 & 1 \\ -1 & 1 & 0 \end{bmatrix} \quad \mathbf{A}_2 = \begin{bmatrix} -1 & 1 & 0 & 1 \\ 1 & -1 & 1 & 0 \\ 0 & 0 & -1 & 0 \end{bmatrix}$$

$$\mathbf{Q}_t = \mathbf{A}_1^{-1} \mathbf{A} = \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 & -1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 0 & -1 & 0 \end{bmatrix}$$

$$\mathbf{Q}_t = \begin{array}{c} (1) \\ (2) \\ (3) \end{array} \begin{array}{c} 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \\ \left| \begin{array}{ccc|ccc} 1 & 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 1 & 0 & -1 & 1 & -1 & 1 \\ 0 & 0 & 1 & 1 & -1 & 1 & 0 \end{array} \right| \end{array}$$


brances ( $\mathbf{U}$ )      co-trees ( $\mathbf{Q}_1$ )

## Second Postulate of Circuit Theory

The fundamental loop matrix of a chosen tree,  $\mathbf{B}_t$  and the vector composed of the element voltages  $\mathbf{v}(\mathbf{t})$  in a given graph G satisfies:

$$\mathbf{B}_t \mathbf{v}(\mathbf{t}) = \mathbf{0}$$

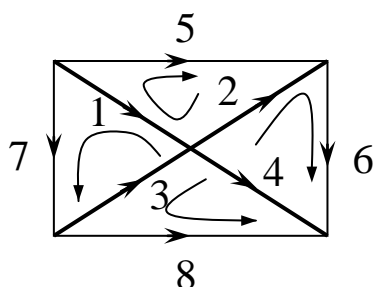which is called *fundamental loop equations*.



$$n_d=5, n_e=8$$

$$\mathbf{B}_t \mathbf{v}(\mathbf{t})=0$$

$$\mathbf{B}_t = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix} \\ \begin{matrix} (5) \\ (6) \\ (7) \\ (8) \end{matrix} & \left| \begin{array}{cccc|cccc} -1 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & -1 & 0 & 0 & 0 & 1 \end{array} \right| \end{matrix}$$

$\underbrace{\hspace{10em}}_{\text{branches (B}_1\text{)}}$

$\underbrace{\hspace{10em}}_{\text{cut-sets (U)}}$

$$\mathbf{v}(\mathbf{t}) = \begin{vmatrix} v_1(t) \\ v_2(t) \\ v_3(t) \\ v_4(t) \\ v_5(t) \\ v_6(t) \\ v_7(t) \\ v_8(t) \end{vmatrix}$$

Fundamental loop equations are given by:

$$(5) \quad -v_1(t) - v_2(t) + v_5(t) = 0$$

$$(6) \quad v_2(t) - v_4(t) + v_6(t) = 0$$

$$(7) \quad -v_1(t) + v_3(t) + v_7(t) = 0$$


$$(8) \quad -v_3(t) - v_4(t) + v_8(t) = 0$$

### Third Postulate of Circuit Theory

The fundamental cut-set matrix of a chosen tree,  $\mathbf{B}_t$  and the vector composed of the element currents  $\mathbf{i}(t)$  in a given graph G satisfies:

$$\mathbf{Q}_t \mathbf{i}(t) = \mathbf{0}$$

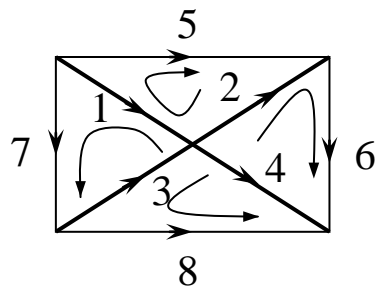which is called *fundamental cut-set equations*.



$$n_d=5, n_e=8$$

$$\mathbf{Q}_t \mathbf{i}(t) = \mathbf{0}$$

$$\mathbf{Q}_t = \begin{matrix} & & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ \begin{matrix} (1) \\ (2) \\ (3) \\ (4) \end{matrix} & \left| \begin{array}{cccc|cccc} 1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 \end{array} \right| \end{matrix} \quad \mathbf{i}(t) = \left| \begin{array}{c} i_1(t) \\ i_2(t) \\ i_3(t) \\ i_4(t) \\ i_5(t) \\ i_6(t) \\ i_7(t) \\ i_8(t) \end{array} \right|$$

$\underbrace{\hspace{10em}}_{\text{branches (B}_1\text{)}}$ 
 $\underbrace{\hspace{10em}}_{\text{cut-sets (U)}}$

fundamental cut-set equations are given by:

$$(1) \quad i_1(t) + i_5(t) + i_7(t) = 0$$

$$(2) \quad i_2(t) + i_5(t) - i_6(t) = 0$$

$$(3) \quad i_3(t) - i_7(t) + i_8(t) = 0$$

$$(4) \quad i_4(t) + i_6(t) + i_8(t) = 0$$

Since  $\mathbf{Q}_t = \mathbf{A}_1^{-1} \mathbf{A}$


$$\mathbf{Q}_t \mathbf{i}(t) = \mathbf{0} \quad \Leftrightarrow \quad \mathbf{A} \mathbf{i}(t) = \mathbf{0}$$

$$\underbrace{\begin{bmatrix} \mathbf{A}_1 & \mathbf{A}_2 \end{bmatrix}}_{\text{branches (B}_1\text{)}} \underbrace{\begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix}}_{\text{cut-sets (U)}} = \mathbf{0}$$

If we multiply both sides from left with  $\mathbf{A}_1^{-1}$ ,

$$\mathbf{A}_1^{-1} \begin{bmatrix} \mathbf{A}_1 & \mathbf{A}_2 \end{bmatrix} \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} = \begin{bmatrix} \mathbf{U} & \mathbf{A}_1^{-1} \mathbf{A}_2 \end{bmatrix} \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} = \begin{bmatrix} \mathbf{U} & \mathbf{Q}_1 \end{bmatrix} \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} =$$
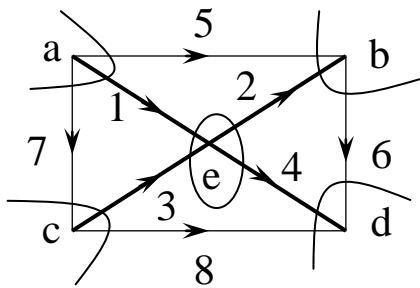
$$\mathbf{Q}_t \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} = \mathbf{Q}_t \mathbf{i}(t) = \mathbf{0}$$



$$\overline{\mathbf{A}} = \begin{array}{c|cccccccc} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ \hline a & 1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ b & 0 & -1 & 0 & 0 & -1 & 1 & 0 & 0 \\ c & 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 \\ d & 0 & 0 & 0 & -1 & 0 & -1 & 0 & -1 \\ e & -1 & 1 & -1 & 1 & 0 & 0 & 0 & 0 \end{array}$$



Reduced incidence matrix,  $\mathbf{A}$

$$\mathbf{A} = \begin{array}{c} \text{a} \\ \text{b} \\ \text{c} \\ \text{d} \end{array} \begin{array}{c|cccc|cccc} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ \hline 1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & -1 & 0 & -1 & 0 & -1 \end{array} \quad \begin{array}{c} \underbrace{\hspace{10em}}_{\mathbf{A}_1} \quad \underbrace{\hspace{10em}}_{\mathbf{A}_2} \end{array}$$

$$\mathbf{i}(\mathbf{t}) = \begin{array}{c} i_1(t) \\ i_2(t) \\ i_3(t) \\ i_4(t) \\ \hline i_5(t) \\ i_6(t) \\ i_7(t) \\ i_8(t) \end{array} = \begin{array}{c} i_1(t) \\ i_2(t) \\ i_3(t) \\ i_4(t) \\ \hline \dot{I}_2(t) \\ i_6(t) \\ i_7(t) \\ i_8(t) \end{array}$$

Incidence equations,  $\mathbf{A} \mathbf{i}(\mathbf{t}) = \mathbf{0}$

$$\begin{array}{ll} \text{(a)} & i_1(t) + i_5(t) + i_7(t) = 0 \\ \text{(b)} & -i_2(t) - i_5(t) + i_6(t) = 0 \\ \text{(c)} & i_3(t) - i_7(t) + i_8(t) = 0 \\ \text{(d)} & -i_4(t) - i_6(t) - i_8(t) = 0 \end{array} \quad \mathbf{A}_1^{-1} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix}$$

$$\mathbf{A}_1^{-1} \mathbf{A}_2 = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 \\ 0 & -1 & 0 & -1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 \\ 0 & 1 & 0 & 1 \end{bmatrix} = \mathbf{Q}_1$$

$$\mathbf{A}_1^{-1} [\mathbf{A}_1 \quad \mathbf{A}_2] \begin{bmatrix} \mathbf{i}_1(\mathbf{t}) \\ \mathbf{i}_2(\mathbf{t}) \end{bmatrix} = [\mathbf{U} \quad \mathbf{A}_1^{-1} \mathbf{A}_2] \begin{bmatrix} \mathbf{i}_1(\mathbf{t}) \\ \mathbf{i}_2(\mathbf{t}) \end{bmatrix} = \mathbf{i}_1(\mathbf{t}) + \mathbf{Q}_1 \mathbf{i}_2(\mathbf{t}) = \mathbf{0}$$

## Tellegen's Theorem

Assume that two different circuits have the same graph  $G$ .

Circuit D

$$\mathbf{B}_t \mathbf{v}(t) = \mathbf{0}$$

$$\mathbf{Q}_t \mathbf{i}(t) = \mathbf{0}$$

( $\mathbf{v}(t), \mathbf{i}(t)$  ile  $\mathbf{v}'(t), \mathbf{i}'(t)$  farklı)

Explicitly,

$$\begin{bmatrix} \mathbf{B}_1 & \mathbf{U} \end{bmatrix} \begin{bmatrix} \mathbf{v}_1(t) \\ \mathbf{v}_2(t) \end{bmatrix} = \mathbf{0}$$

$$\begin{bmatrix} \mathbf{U} & \mathbf{Q}_1 \end{bmatrix} \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} = \mathbf{0}$$

$$\mathbf{v}_2(t) + \mathbf{B}_1 \mathbf{v}_1(t) = \mathbf{0}$$

$$\mathbf{i}_1(t) + \mathbf{Q}_1 \mathbf{i}_2(t) = \mathbf{0}$$

$$\mathbf{v}_2(t) = -\mathbf{B}_1 \mathbf{v}_1(t)$$

$$\mathbf{i}_1(t) = -\mathbf{Q}_1 \mathbf{i}_2(t)$$

Circuit D'

$$\mathbf{B}_t \mathbf{v}'(t) = \mathbf{0}$$

$$\mathbf{Q}_t \mathbf{i}'(t) = \mathbf{0}$$

$$\begin{bmatrix} \mathbf{B}_1 & \mathbf{U} \end{bmatrix} \begin{bmatrix} \mathbf{v}'_1(t) \\ \mathbf{v}'_2(t) \end{bmatrix} = \mathbf{0}$$

$$\begin{bmatrix} \mathbf{U} & \mathbf{Q}_1 \end{bmatrix} \begin{bmatrix} \mathbf{i}'_1(t) \\ \mathbf{i}'_2(t) \end{bmatrix} = \mathbf{0}$$

$$\mathbf{v}'_2(t) + \mathbf{B}_1 \mathbf{v}'_1(t) = \mathbf{0}$$

$$\mathbf{i}'_1(t) + \mathbf{Q}_1 \mathbf{i}'_2(t) = \mathbf{0}$$

$$\mathbf{v}'_2(t) = -\mathbf{B}_1 \mathbf{v}'_1(t)$$

$$\mathbf{i}'_1(t) = -\mathbf{Q}_1 \mathbf{i}'_2(t)$$

$$\mathbf{v}^T(t) \mathbf{i}(t) = \begin{bmatrix} \mathbf{v}_1^T(t) & \mathbf{v}_2^T(t) \end{bmatrix} \begin{bmatrix} \mathbf{i}_1(t) \\ \mathbf{i}_2(t) \end{bmatrix} = \mathbf{v}_1^T(t) \mathbf{i}_1(t) + \mathbf{v}_2^T(t) \mathbf{i}_2(t) =$$

$$\mathbf{v}_1^T(t) [-\mathbf{Q}_1 \mathbf{i}_2(t)] + [-\mathbf{v}_1^T(t) \mathbf{B}_1^T] \mathbf{i}_2(t) =$$

$$\mathbf{v}_1^T(t) \mathbf{B}_1^T \mathbf{i}_2(t) - \mathbf{v}_1^T(t) \mathbf{B}_1^T \mathbf{i}_2(t) = \mathbf{0} \quad (\mathbf{Q}_1 = -\mathbf{B}_1^T)$$

Thus  $\mathbf{v}^T(t) \mathbf{i}(t) \equiv \mathbf{0}$

Similarly, we can deduce the followings for the circuit D'

$$\mathbf{v}'^T(\mathbf{t}) \mathbf{i}'(\mathbf{t}) \equiv \mathbf{0}$$

$$\mathbf{v}^T(\mathbf{t}) \mathbf{i}'(\mathbf{t}) \equiv \mathbf{0}$$

$$\mathbf{v}'^T(\mathbf{t}) \mathbf{i}(\mathbf{t}) \equiv \mathbf{0}$$

From these expressions, we can obtain the following property:

In an electrical circuit, the sum of instantaneous power equals zero,

$$\text{i.e. } p(t) = \mathbf{v}(\mathbf{t})^T \mathbf{i}(\mathbf{t}) = \sum_{k=1}^{n_e} \mathbf{v}_{\mathbf{k}}(\mathbf{t}) \mathbf{i}_{\mathbf{k}}(\mathbf{t}) \equiv \mathbf{0}$$

Energy generated = energy dissipated  
(the law of conservation of energy)